MyElectronicProjects Documentation

Release 0.0.0

ponty

CONTENTS

1	About	2
2	Stripboard design	3
3	audio_amplifier 3.1 Schematic 3.2 Board 3.3 Partlist 3.4 3D view 3.5 Sources	4 4 4 5 6 8
4	Wire bending tool 4.1 Image 4.2 Board 4.3 3D view	9 9 10
5	5.1 Test on Ubuntu	12 12 13 13 13
6		14 14
7	7.1 Images	15 15 16
8	8.1 Images	17 17 17
9	9.1 Images 9.2 Schematic 9.3 Board 9.4 Partlist 9.5 3D view 9.5 3D view	19 21 21 23 24 26
10		27 27

Board	27
Partlist	29
3D view	29
Images	31
200 AVR programmer	33
Test on Übuntu	33
Image	33
Schematic	35
Board	35
Partlist	37
3D view	38
Sources	40
asp AVR programmer	41
V-USB hardware recommendation	41
Makefile	42
Test on Ubuntu	42
Schematic	43
Board	43
	45
3D view	46
Reset	48
Sources	49
LED	50
	Partlist 3D view Images 200 AVR programmer Test on Ubuntu Image Schematic Board Partlist 3D view Sources asp AVR programmer V-USB hardware recommendation Makefile Test on Ubuntu Schematic Board Partlist 3D view Reset Sources

MyElectronicProjects

Date March 12, 2012

PDF MyElectronicProjects.pdf

CONTENTS 1

CHAPTER

ONE

ABOUT

Hobby electronic projects built by me.

Most of them are built on stripboard.

Links:

• home: https://github.com/ponty/MyElectronicProjects

• documentation: http://ponty.github.com/MyElectronicProjects

Design tool: EAGLE Light Edition

STRIPBOARD DESIGN

Stripboard design representation in eagle:

- holes: copper should be cut or drilled here
- SMD: through-hole component, legs are drawn on top layer
- top layer: wires
- lines on documentation layer: wires
- bottom layer: original parallel strips of copper, only those are drawn, which are used for connection
- via: soldering points


Some components have no 3D view in the documentation.

AUDIO_AMPLIFIER

Status: under construction


It is used for ...


3.1 Schematic

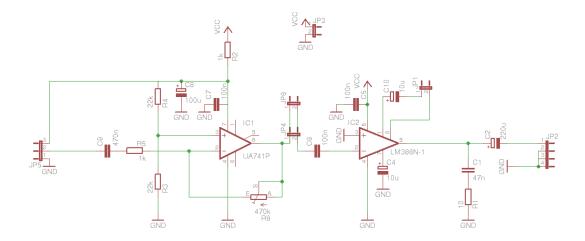


3.2 Board

Normal, bottom mirrored, wires only:

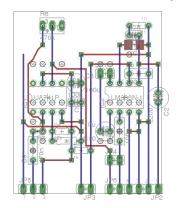

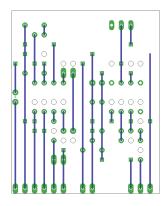

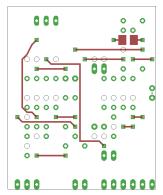

3.3 Partlist

Table 3.1:

part	value	position
C1	47n	(1.45 1.7)
C2	220u	(1.7 1.05)
C4	10u	(1.45 1.6)
C5	100n	(1.5 1.3)
C6	100n	(1.3 0.7)
C7	100n	(0.85 1)
C8	100u	(0.85 1.2)
C9	470n	(0.4 0.5)
C10	10u	(1.15 0.7)
IC1	UA741P	(0.55 1.05)
IC2	LM386N-1	(1.35 1.05)
JP1		(1.15 1.3)
JP2		(1.55 0.1)
JP3		(0.95 0.1)
JP4		(1.25 0.4)
JP5		(0.4 0.1)
JP6		(1.25 0.1)
R1	10	(1.5 1.8)
R2	1k	(0.9 0.5)
R3	22k	(0.75 0.6)
R4	22k	(0.7 0.7)
R5	1k	(0.45 0.7)
R6	470k	(0.6 1.8)

3.3. Partlist 5


3.4 3D view

3.4.1 Front




3.4. 3D view 6

3.4.2 Right side

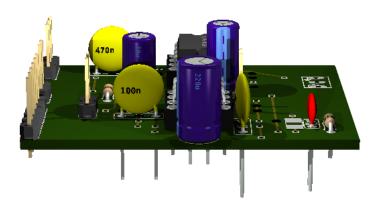


3.4.3 Left side

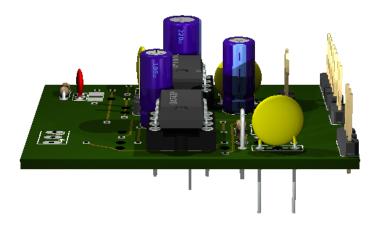

3.4. 3D view 7

3.4.4 Bottom

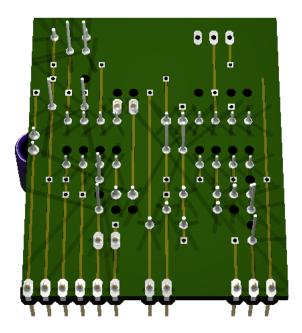

3.5 Sources

original design


3.5. Sources 8

WIRE BENDING TOOL

Status: OK


It is used for bending wires.

4.1 Image

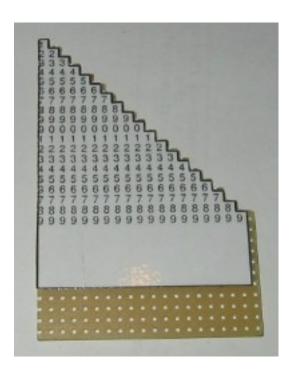


4.2 Board

Normal:

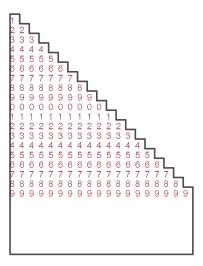

4.3 3D view

4.3.1 Front

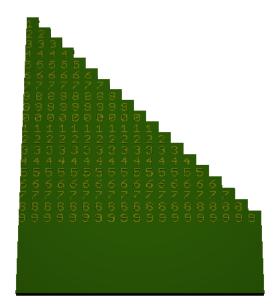

4.3. 3D view 10

4.3.2 Right side



4.3. 3D view 11

DAPA AVR PROGRAMMER


Status: OK

It is used for programming AVR controller and Arduino compatible boards using the parallel port.


5.1 Test on Ubuntu

checking:

5.2 Image

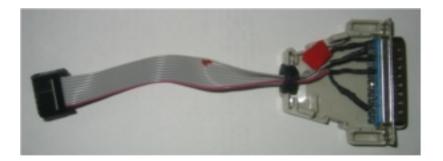

5.3 Schematic

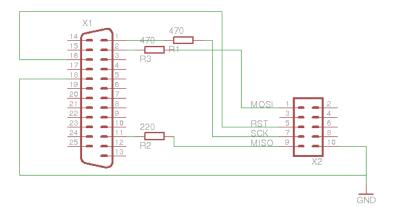

5.4 Partlist

Table 5.1:

part	value
R1	470
R2	220
R3	470
X1	
X2	

5.5 Sources

original design

Parallel port specification

ISP pinout

5.3. Schematic

FTDI CABLE

Status: OK Special cable.

connections:

FTDI pin	signal	color	6p4c (RJ14) pin
1	gnd	red	4
2	cts		
3	5v	green	3
4	rxd	yellow	2
5	txd	black	5
6	rts		

standard color code is reversed

6.1 Sources

RJ14 pinout

RJ14 wiring details

GARMIN ETREX DATA CABLE

Status: OK

It is used for connecting Garmin eTrex to the serial port.

connections:

DB9 pin	garmin pin
3 (TxD)	2 (In)
2 (RxD)	3 (Out)
5 (GND)	4 (GND)

7.1 Images





7.2 Sources

original design

7.2. Sources 16

SERIAL PORT LOOPBACK

Status: OK

It is used for testing the serial port.

Connected pins:

- 1-6-4
- 2-3
- 7-8

8.1 Images



8.2 Sources

original design

Serial port pinout


8.2. Sources 18


PARALLEL PORT MONITOR

Status: OK

It is used for monitoring the parallel port signals.


9.1 Images

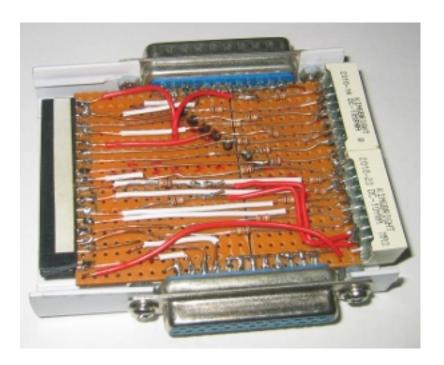


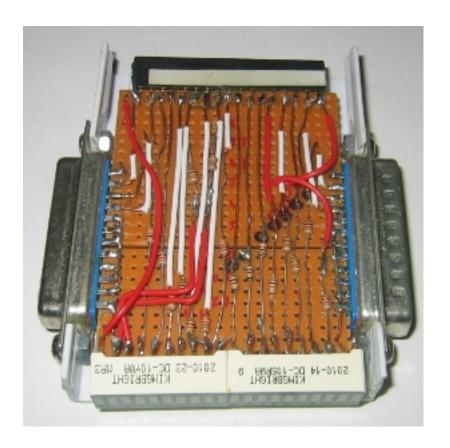



9.1. Images 20

9.2 Schematic

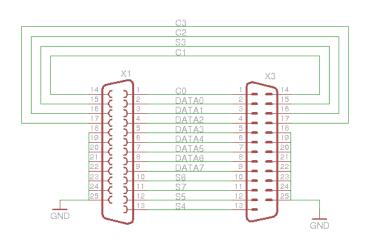

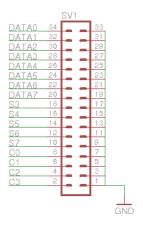

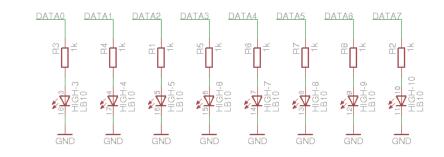


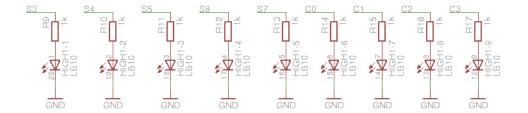



9.3 Board

Normal, bottom mirrored, wires only:

9.2. Schematic 21

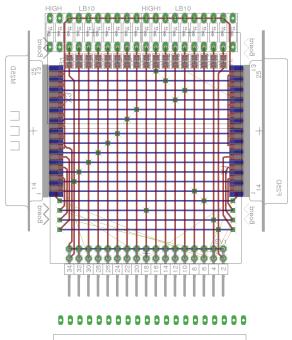

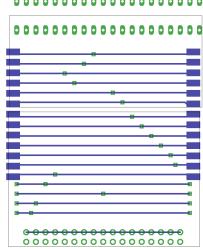

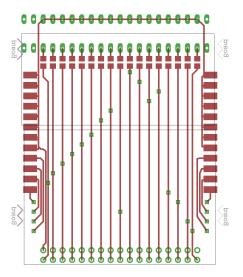

9.3. Board 22

9.4 Partlist


Table 9.1:

part	value	position
HIGH	LB10	(0.45 2.55)
HIGH1	LB10	(1.45 2.55)
R1	1k	(0.4 2.25)
R2	1k	(0.9 2.25)
R3	1k	(0.2 2.25)
R4	1k	(0.3 2.25)
R5	1k	(0.5 2.25)
R6	1k	(0.6 2.25)
R7	1k	(0.7 2.25)
R8	1k	(0.8 2.25)
R9	1k	(1 2.25)
R10	1k	(1.1 2.25)
R11	1k	(1.2 2.25)
R12	1k	(1.3 2.25)
R13	1k	(1.4 2.25)
R14	1k	(1.5 2.25)
R15	1k	(1.6 2.25)
R16	1k	(1.7 2.25)
R17	1k	(1.8 2.25)
SV1		(1 0.25)
X1		(2.175 1.525)
X3		(-0.175 1.525)

9.4. Partlist

9.5 3D view

9.5.1 Front

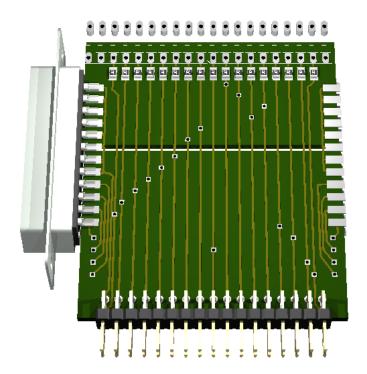


9.5. 3D view 24

9.5.2 Right side




9.5.3 Left side

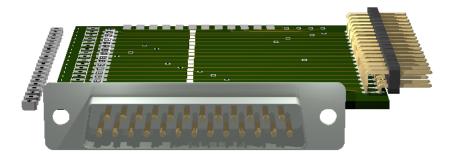

9.5. 3D view 25

9.5.4 Bottom

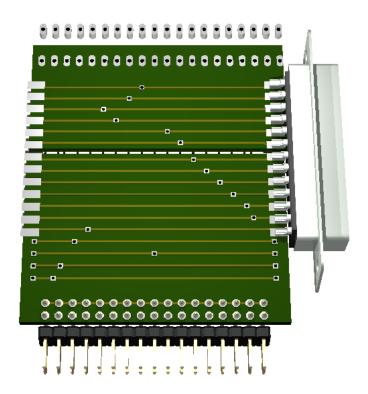

9.6 Sources

original idea


9.6. Sources 26

SERIAL PORT MONITOR

Status: OK


On each signal there is one LED for positive and one LED for negative voltage. It is easy to change connections or connect external parts. Examples: Loop-Back, Null Modem,..


10.1 Schematic

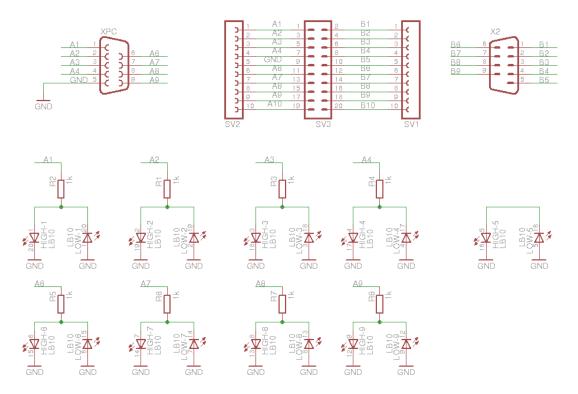


10.2 Board

Normal, bottom mirrored, wires only:

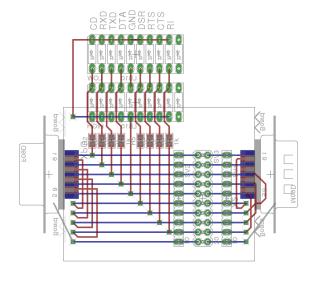

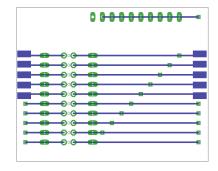

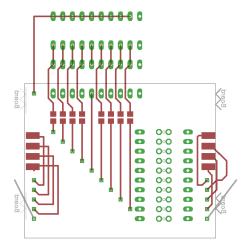

10.2. Board 28


10.3 Partlist

Table 10.1:

part	value	position
HIGH	LB10	(0.75 1.65)
LOW	LB10	(0.75 2.15)
R1	1k	(0.4 1.25)
R2	1k	(0.3 1.25)
R3	1k	(0.5 1.25)
R4	1k	(0.6 1.25)
R5	1k	(0.8 1.25)
R6	1k	(0.9 1.25)
R7	1k	(1 1.25)
R8	1k	(1.1 1.25)
SV1		(1.7 0.65)
SV2		(1.2 0.65)
SV3		(1.45 0.65)
X2		(2.15 0.9)
XPC		(-0.15 0.9)


10.4 3D view

10.4.1 Front

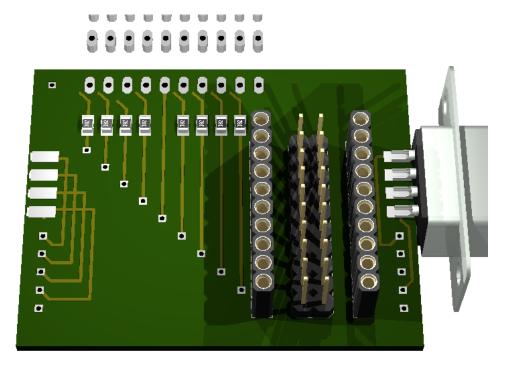


10.3. Partlist

10.4.2 Right side

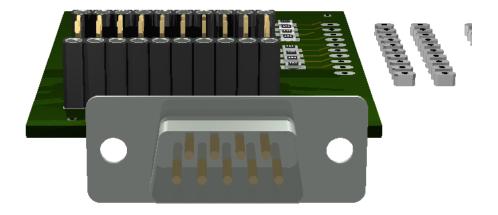


10.4.3 Left side

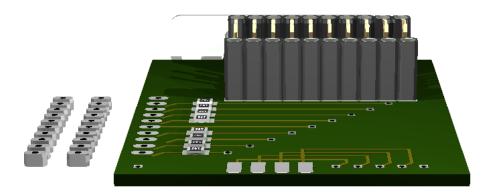


10.4. 3D view 30


10.4.4 Bottom

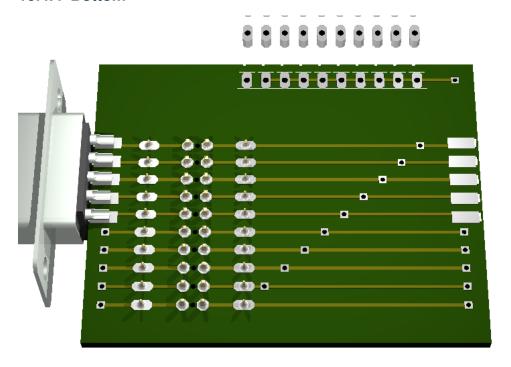

10.5 Images

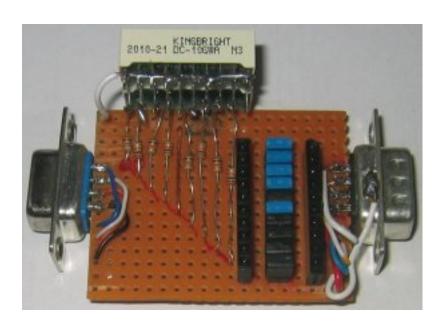

10.5. Images 31

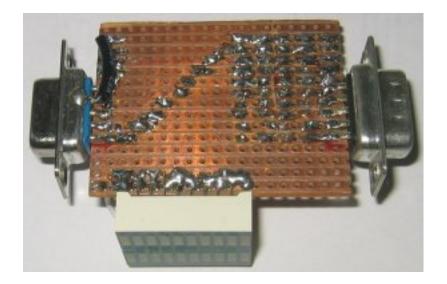

10.5. Images 32

STK200 AVR PROGRAMMER


Status: OK


It is used for programming AVR controller and Arduino compatible boards using the parallel port.

11.1 Test on Ubuntu

checking:


11.2 Image

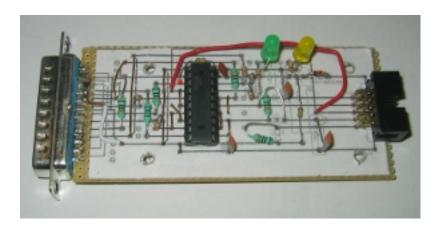

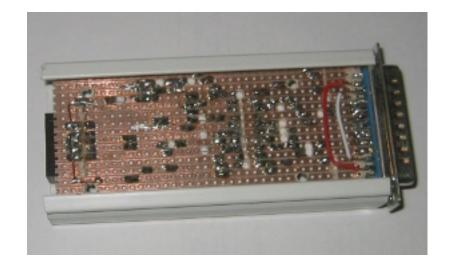

11.2. Image 34


11.3 Schematic

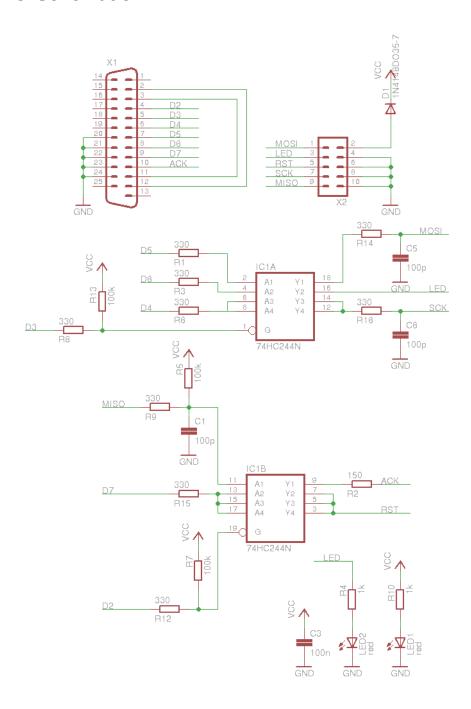


11.4 Board

Normal, bottom mirrored, wires only:

11.3. Schematic 35

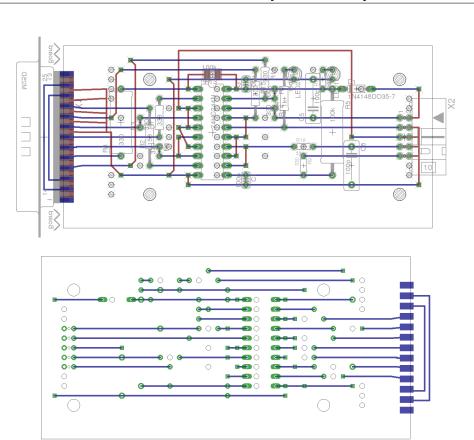

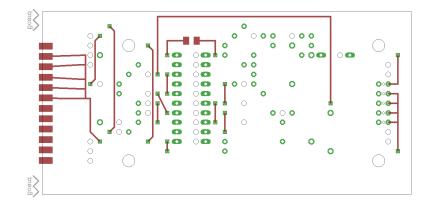

11.4. Board 36

11.5 Partlist


Table 11.1:

part	value	position
C1	100p	(2.3 0.95)
C3	100n	(2.3 1.95)
C5	100p	(3 1.8)
C6	100p	(3.4 1.1)
D1	1N4148DO35-7	(3.45 1.9)
IC1	74HC244N	(1.95 1.45)
LED1	red	(3.2 2.05)
LED2	red	(2.8 2.05)
R1	330	(1.4 1.6)
R2	150	(1.3 1.4)
R3	330	(1.2 1.55)
R4	1k	(2.7 1.8)
R5	100k	(3.2 1.45)
R6	330	(1.4 1.25)
R7	100k	(2.6 1.85)
R8	330	(1 1.55)
R9	330	(2.9 1.1)
R10	1k	(3.1 2)
R12	330	(2.5 2)
R13	100k	(1.95 2.05)
R14	330	(2.6 1.65)
R15	330	(2.4 1.85)
R16	330	(2.9 1.3)
X1		(0.2 1.4)
X2		(3.95 1.4)

11.5. Partlist


11.6 3D view

11.6.1 Front

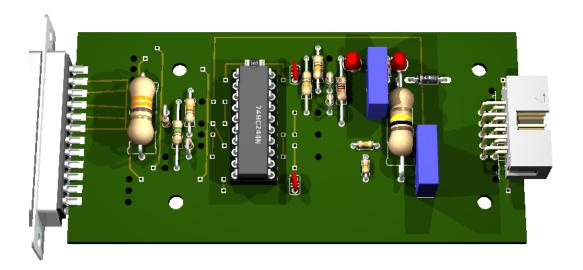


11.6. 3D view 38

11.6.2 Right side

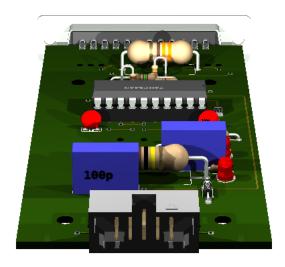


11.6.3 Left side

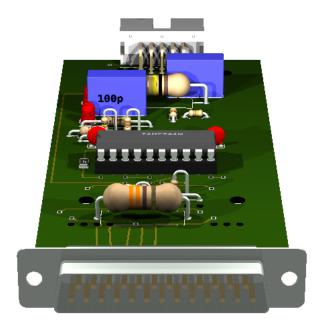

11.6. 3D view 39

11.6.4 Bottom

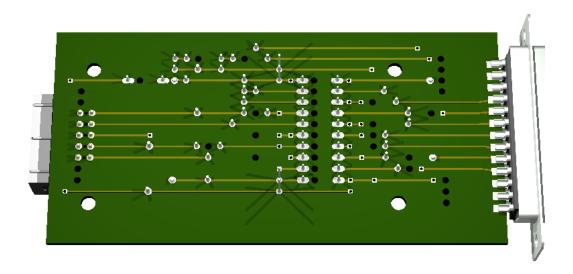

11.7 Sources

original design

Parallel port specification

ISP pinout

similar designs:

• http://www.sbprojects.com/projects/stk200/

11.7. Sources 40

USBASP AVR PROGRAMMER

Status: OK

It is used for programming AVR controller and Arduino compatible boards using the USB port.

firmware, design: http://www.fischl.de/usbasp/

USBasp is based on V-USB (http://www.obdev.at/products/vusb/index.html)

12.1 V-USB hardware recommendation

only difference to USBasp: $1.5 \text{ k}\Omega$ pull-up resistor

http://vusb.wikidot.com/hardware

"Solution B: Level conversion on D+ and D- Level conversion with Zener diodes.

Instead of reducing the AVR's power supply, we can limit the output voltage on D+ and D- with Zener diodes. We recommend 3.6 V low power types, those that look like 1N4148 (usually 500 mW or less). Low power types are required because they have less capacitance and thus cause less distortion on the data lines. And 3.6 V is better than 3.3 V because 3.3 V diodes yield only ca. 2.7 V in conjunction with an 1.5 k Ω (or more exactly 10 k Ω) pull-up resistor. With 3.3 V diodes, the device may not be detected reliably.

If you use Zener diodes for level conversion, please measure the voltage levels to make sure that the diodes you have chosen match the requirements.

Advantages of the Zener diode approach:

- Low cost.
- Easy to obtain.
- Entire design can be at 5 V.
- AVR can be clocked at high rates.

Disadvantages:

- Not a clean solution, a compromise between all parameters must be found.
- Zener diodes come with a broad range of characteristics, especially at low currents, results may not be reproducible.
- High currents when sending high-level.
- High level is different for signaling and in idle state because signaling uses high currents to drive the diodes while idle state is driven by a 1.5 k Ω pull-up resistor."

12.2 Makefile

Tested with atmega88. Makefile settings:

```
TARGET=atmega88
HFUSE=0xdd
LFUSE=0xef
```

12.3 Test on Ubuntu

```
checking:
```

```
$ lsusb |grep -i 16c0:05dc
Bus 003 Device 006: ID 16c0:05dc VOTI shared ID for use with libusb
$ ls -l /dev/bus/usb/003/006
crw-rw-r-- 1 root root 189, 261 2011-11-05 10:31 /dev/bus/usb/003/006
$ avrdude -patmega88 -cusbasp
avrdude: Warning: cannot query manufacturer for device: error sending control message: Operation avrdude: error: could not find USB device "USBasp" with vid=0x16c0 pid=0x5dc

The permission should be changed:
$sudo nano /etc/udev/rules.d/60-objdev.rules
add this line:

ATTRS{idVendor}=="16c0", ATTRS{idProduct}=="05dc", GROUP="users", MODE="0666"
```

update rules:

\$sudo udevadm trigger


checking again:

Permission is OK now.

Testing with connected controller:


12.2. Makefile 42

12.4 Schematic

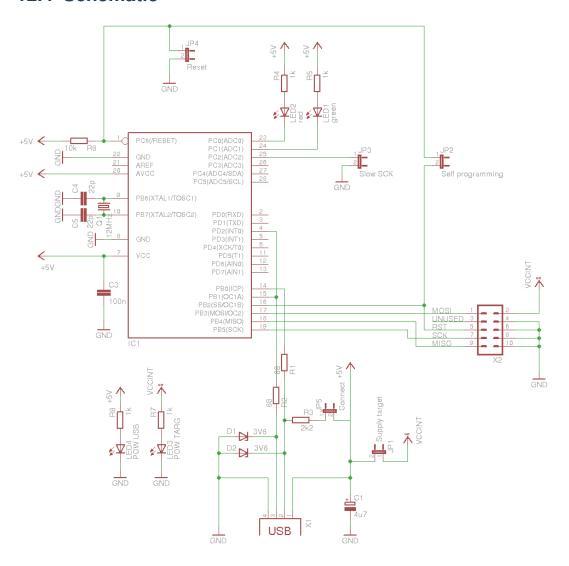



12.5 Board

Normal, bottom mirrored, wires only:

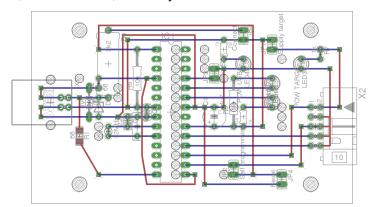

12.4. Schematic 43

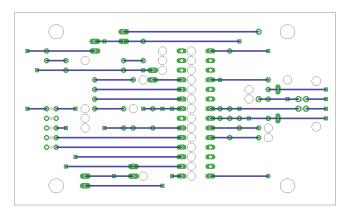

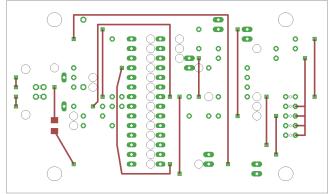

12.5. Board 44

12.6 Partlist


Table 12.1:

part	value	position
C1	4u7	(2.4 0.8)
C3	100n	(1.7 0.85)
C4	22p	(1.5 0.75)
C5	22p	(1.6 0.7)
D1	3V6	(1.1 0.95)
D2	3V6	(1.2 0.9)
IC1		(1.95 0.85)
JP1	Supply target	(3 1.55)
JP2	Self programming	(2.6 0.25)
JP3	Slow SCK	(2.4 1.25)
JP4	Reset	(3.1 0.15)
JP5	Connect	(2.7 1.65)
LED1	green	(3 1.15)
LED2	red	(3 0.95)
LED3	POW TARG	(3.3 1.35)
LED4	POW USB	(2.7 1.35)
Q1	12MHz	(1.3 0.65)
R1	68	(1 0.6)
R2	68	(1.2 1.15)
R3	2k2	(1.3 1.35)
R4	1k	(2.7 0.8)
R5	1k	(2.6 0.95)
R6	10k	(1.6 1.2)
R7	1k	(3.5 1.45)
R8	1k	(2.5 1.5)
X1		(0.7 0.95)
X2		(3.45 0.7)

12.6. Partlist 45


12.7 3D view

12.7.1 Front

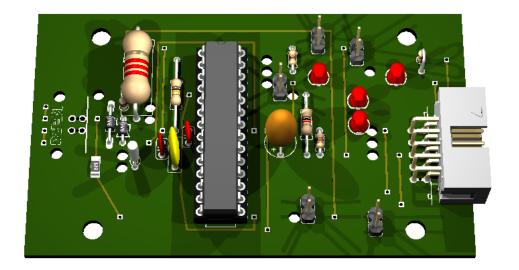


12.7. 3D view 46

12.7.2 Right side

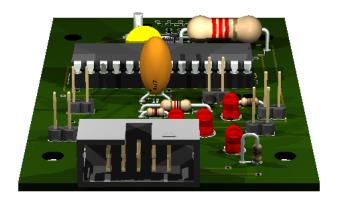


12.7.3 Left side

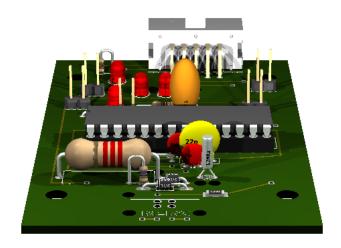

12.7. 3D view 47

12.7.4 Bottom

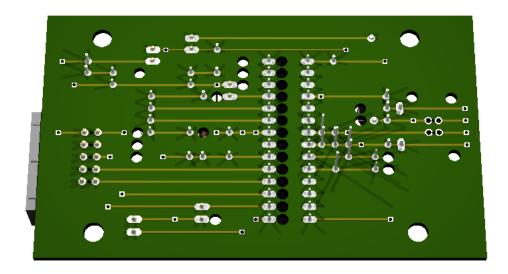

12.8 Reset

To reset on Ubuntu:

```
#!/usr/bin/env python
import logging
import usb.core
logging.basicConfig(level=logging.DEBUG)
import fcntl
ID_VENDOR = 0x16c0
ID\_PRODUCT = 0x05dc
USBDEVFS_RESET = 21780
def find():
    print("searching for device (%x:%x)" % (ID_VENDOR, ID_PRODUCT))
    dev = usb.core.find(idVendor=ID_VENDOR,
                        idProduct=ID_PRODUCT,
    if not dev:
       print("device not found")
    return dev
def usbstr(i):
    s=str(i)
    s='000'[0:3-len(s)]+s
```

12.8. Reset 48

```
return s
def usbfs_filename(dev):
    return '/dev/bus/usb/%s/%s' % (usbstr(dev.bus), usbstr(dev.address))
def reset1(dev):
   fname=usbfs_filename(dev)
   print("Resetting USB device %s" % fname)
    with open(fname, 'w') as fd:
       rc = fcntl.ioctl (fd, USBDEVFS_RESET, 0)
        if (rc < 0):
           print("Error in ioctl")
    print("OK")
def reset2(dev):
   dev.reset() # not working
dev=find()
if dev:
    reset1(dev)
```

12.9 Sources

original design

ISP pinout

similar projects:

• http://lategahn.2log.de/index.php?USBASP-Stripboard-layout

12.9. Sources 49

CHAPTER THIRTEEN

USB LED

Status: OK

It is used for testing USB power.



